



Introduction to VHDL

Introduction to HDL

- In electronics, HDL is a class of computer language for the formal description of the electronic circuit.
- It is used to model the circuit at different levels.
- (Top level to gate level).
- A synthesizable HDL code results to an equivalent hardware.
- HDL can be used for verification of the circuits.


Classification of HDL

VHDL (VHSIC-HDL)	Verilog
It is strongly typed	It is weakly typed
High verbosity	Low verbosity
Case insensitive	Case sensitive
Non C like	More C like
Upto gate level implementation only	Transistor level implementation is possible

Features of VHDL

- Supports concurrent and sequential execution of statements.
- It possesses IEEE standards.
- Like C, VHDL also supports different data types, conditional, relational, logical, arithmetic operators.
- Supports 3 different modelling styles
 1. Dataflow
 2. Behavioural
 3. Structural

Different Modelling Style

 

Operators

LOGICAL :

- AND
- OR
- NOR
- NAND
- NOT
- XOR
- XNOR

ARITHMETIC:

- + addition
- - subtraction
- * multiplication
- / division
- ABS absolute value
- MOD modulus
- REM remainder
- ** exponent

Comparison Operators:

- = equal to
- /= not equal to
- < less than
- > greater than
- <= less than or equal to
- >= greater than or equal to

Branching Statements:

```
if condition_1 then  
    sequential statements  
elsif condition2 then  
    sequential statements  
else  
    sequential statements  
end if;
```

Branching Statements:

```
case expression is  
    when choice =>  
        sequential statements  
    when choice =>  
        sequential statements  
end case;
```

Looping Statements

```
optional_label: for parameter in range loop  
    sequential statements  
end loop label;
```

Ex:

```
for I in 1 to 10 loop  
    if (REPEAT = '1') then  
        I := I-1; -- Illegal  
    end if;  
end loop;
```




Looping Statements

```
while condition loop  
    sequential statements  
end loop;
```

Circuit 1



A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

VHDL Dataflow Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

architecture dataflow of
circuit_1 is
    Begin
        S <= A xor B;
        C <= a and b;
end dataflow;
```

VHDL Behavioral Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

architecture behavior of circuit_1 is
    Begin
        c1: process (A,B)
        Begin
            if A = '1' then
                S <= not B;
                C <= B;
            Else
                S <= B;
                C <= '0';
            end if;
        end process c1;
    end behavior;
```

VHDL Structural Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;


entity circuit_1 is                                -- Entity declaration for circuit_1
port (A, B: in std_logic;
      S, C: out std_logic);
end circuit_1;

architecture structure of circuit_1 is            -- Architecture body for circuit_1
component xor_gate                                -- xor component declaration
  port (i1, i2: in std_logic;
        o1: out std_logic);
end component;

component and_gate                                -- and component declaration
  port (i3, i4: in std_logic;
        o2: out std_logic);
end component;
```


VHDL Structural Modelling Style
 
```
begin
  u1: xor_gate port map (i1 => A, i2 => B, o1 => S);
  u2: and_gate port map (i3 => a, i4 => b, o2 => C);
  -- We can also use Positional Association
  --      => u1: xor_gate port map (a, b, sum);
  --      => u2: and_gate port map (a, b, carry_out);
end structure;
```



--Functionality for XOR gate in data flow modelling style

```
library ieee;
use ieee.std_logic_1164.all;

entity xor_gate is
  port (i1, i2: in std_logic;
        o1: out std_logic);
end circuit_1;


architecture dataflow of xor_gate is
  Begin
    o1 <= i1 xor i2;
  end dataflow;
```

--Functionality for AND gate in data flow modelling style

```
library ieee;
use ieee.std_logic_1164.all;


entity and_gate is
  port (i3, i4: in std_logic;
        o2: out std_logic);
end circuit_1;

 architecture dataflow of and_gate is
  Begin
    o2 <= i3 and i4;
  end dataflow;
```



Test Bench

 - Used for verification of the design
- HDL code with no port list and non synthesizable constructs.
- The main objectives of Test Bench is to:
 - 1.Instantiate the design under test (DUT)
 - 2.Generate stimulus waveforms for DUT
 - 3.Generate reference outputs and compare them with the outputs of DUT
 - 4.Automatically provide a pass or fail indication




VHDL Test Bench for Circuit 1

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY circuit_1_tb IS
END circuit_1_tb;

ARCHITECTURE circuit_1_tb OF circuit_1_tb IS

 COMPONENT circuit1
  PORT (
    A : IN  bit;
    B : IN  bit;
    S : OUT bit;
    C : OUT bit;
  );
END COMPONENT;
```



```
-- input test signals and resulting output signals from DUT to be
                        declared
```

```
signal a_tb : bit := '0';
signal b_tb : bit := '0';
signal s_tb : bit;
signal c_tb : bit;
```

```
BEGIN
```

```
uut: circuit1 PORT MAP
```

```
(
```

```
    A => a_tb,
```

```
    B => b_tb,
```

```
    S => s_tb,
```

```
    C => c_tb
```

```
);
```

```
-- instantate the DUT with  
-- structural modelling style
```

```
Process
```

```
    Begin
```

```
        a_tb <= '0'; b_tb <= '0';
```

```
        wait for 50 ns;
```

```
        a_tb <= '0'; b_tb <= '1';
```

```
        wait for 50 ns;
```

```
        a_tb <= '1'; b_tb <= '0';
```

```
        wait for 50 ns;
```

```
        a_tb <= '1'; b_tb <= '1';
```





```
        wait;
```


```
end process;
```

```
--apply the stimulus with  
--behavioural modelling style
```

```
END circuit_1_tb ;
```

Simulation Results of Circuit 1

Name	Value	0 ns	50 ns	100 ns	150 ns
 a	1				
 b	1				
 s	0				
 c	1				

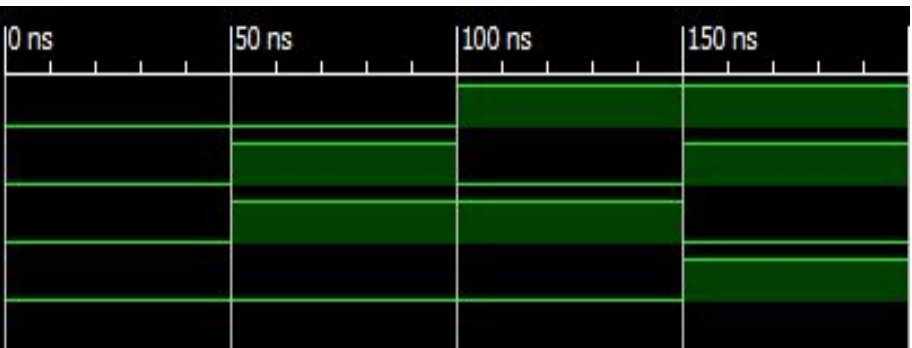

INPUT AND OUTPUT PINS DETAILS OF MAX 3000A

Inputs	Pin No.
SW1	4
SW2	5
SW3	6
SW4	8
SW5	9
SW6	11
SW7	12
SW8	14


Outputs	Pin No.
LED1	24
LED 2	25
LED 3	26
LED 4	27
LED 5	28
LED 6	29
LED 7	31
LED 8	33

Configuring Helium Board using JTAG

1. Open terminal -> JTAG
2. cable ft2232 vid=0x0403 pid=0x6010
3. detect
- 4.svf “file path.svf”



VHDL Question Batch -1

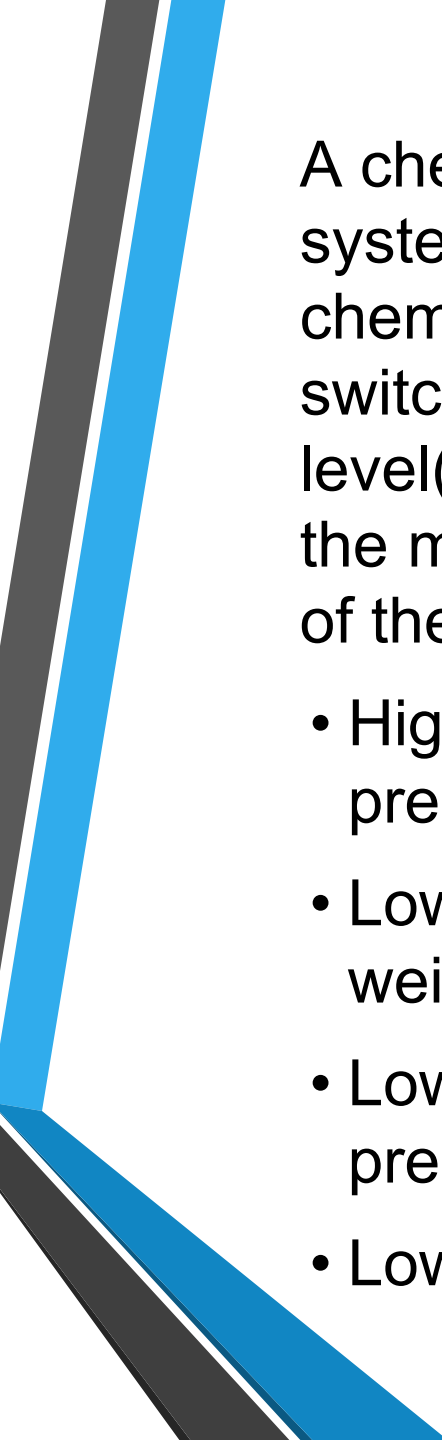


A chemical plant needs a microprocessor driven alarm system to warn of critical conditions in one of its chemical tanks, The tank has four HIGH/LOW (1/0) switches that monitor temperature(T), pressure(P) fluid level(L)and weight(W). Design a system that will notify the microprocessor to activate an alarm when any one of the following condition arise:-

- High fluid level with high temperature and high pressure
- Low fluid level with high temperature and high weight.
- Low fluid level with Low temperature and high pressure
- Low fluid level with high temperature and low weight



VHDL Question Batch -2

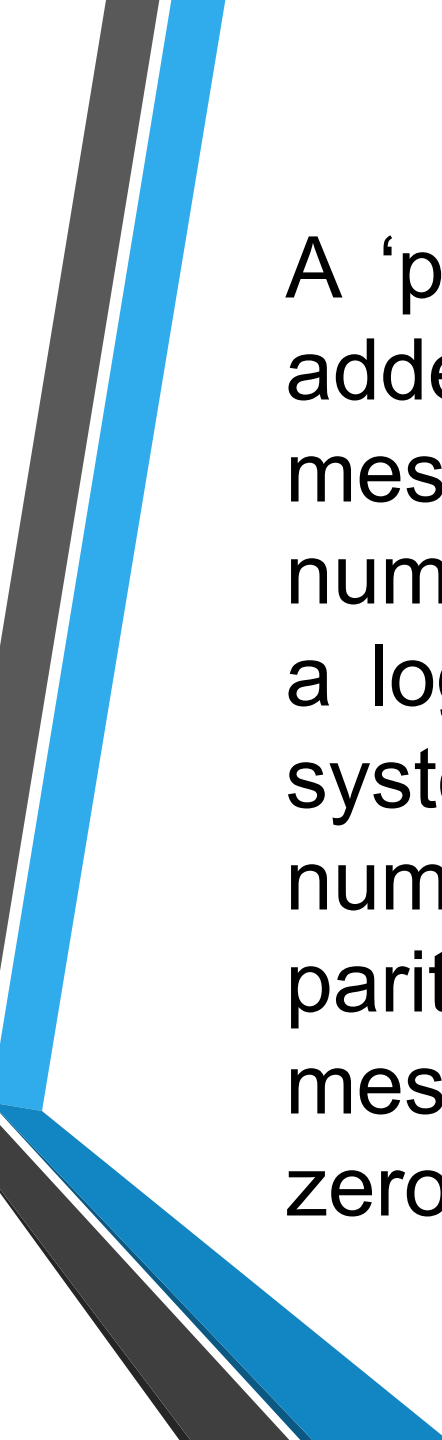

A 'parity bit' is an additional bit that is added to aid error detection in a digital message. It is calculated based on the numbers of 1's in any message. Design a logic that generates a parity bit for a system that deals with 4-bit binary numbers. The logic should produce the parity bit as '1' if the number of 1's in the message is even, otherwise generates zero.